

Task 19
CMOS layout of AND gate
Group 6

